



**ASSIGNMENT NO : 01**

**CMOS DIGITAL VLSI LAB**


**NAME: MANOJ KUMAR MAHATO**

**ENROLLMENT NO/ROLL NO : MT21MVD014**

**DATE OF SUBMISSION :15/09/2021**

## QUESTION – RC circuit DC analysis

Circuit -

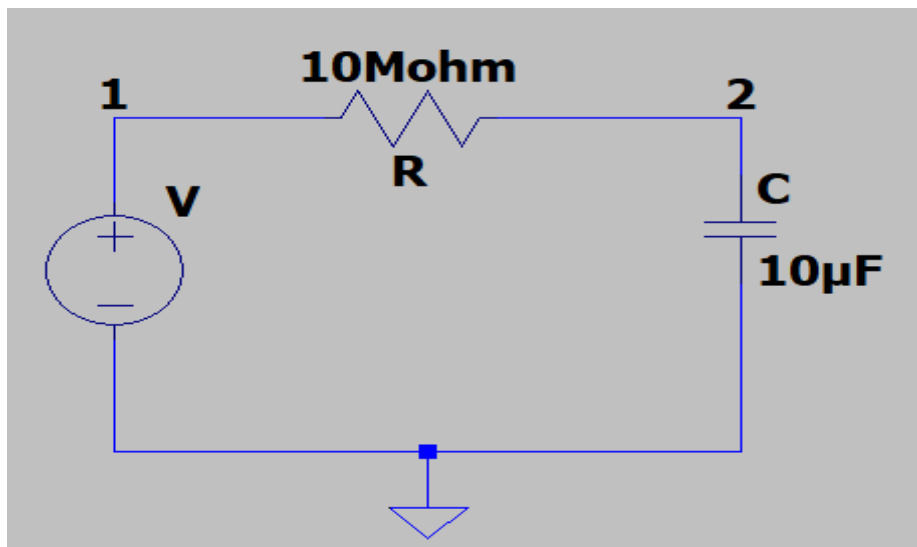

## CODE –

\*RC circuit dc analysis

```
V 1 0 5v
```

```
R 1 2 10M
```

```
C 2 0 10u ic=0
```

```
.control
```

```
dc Vs -4 4 0.1
```

```
run
```

```
plot v(2)
```




```
plot v(1,2)
```

```
plot i(v)
```

```
.endc
```

```
.end
```

## OUTPUT –

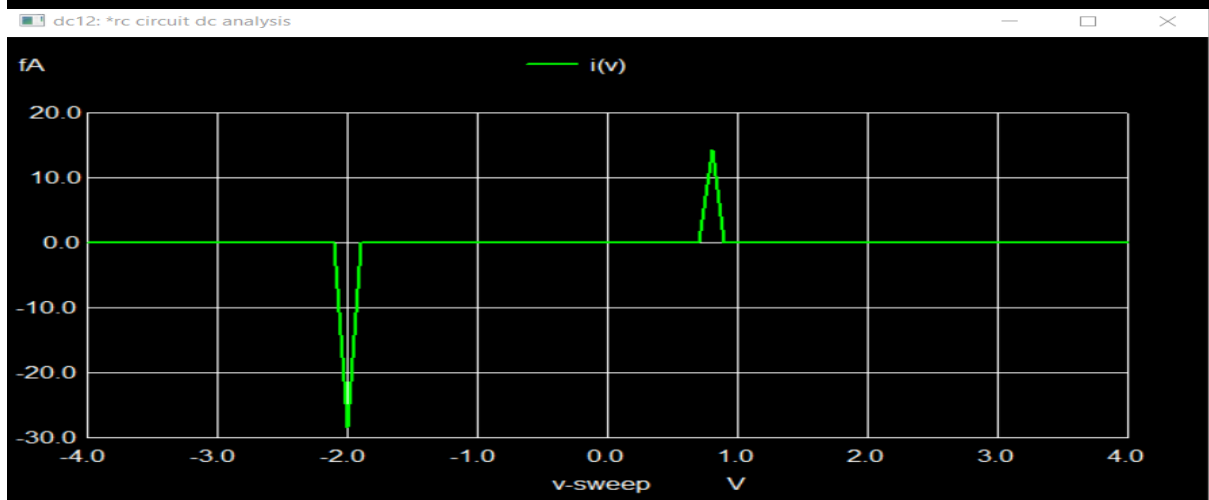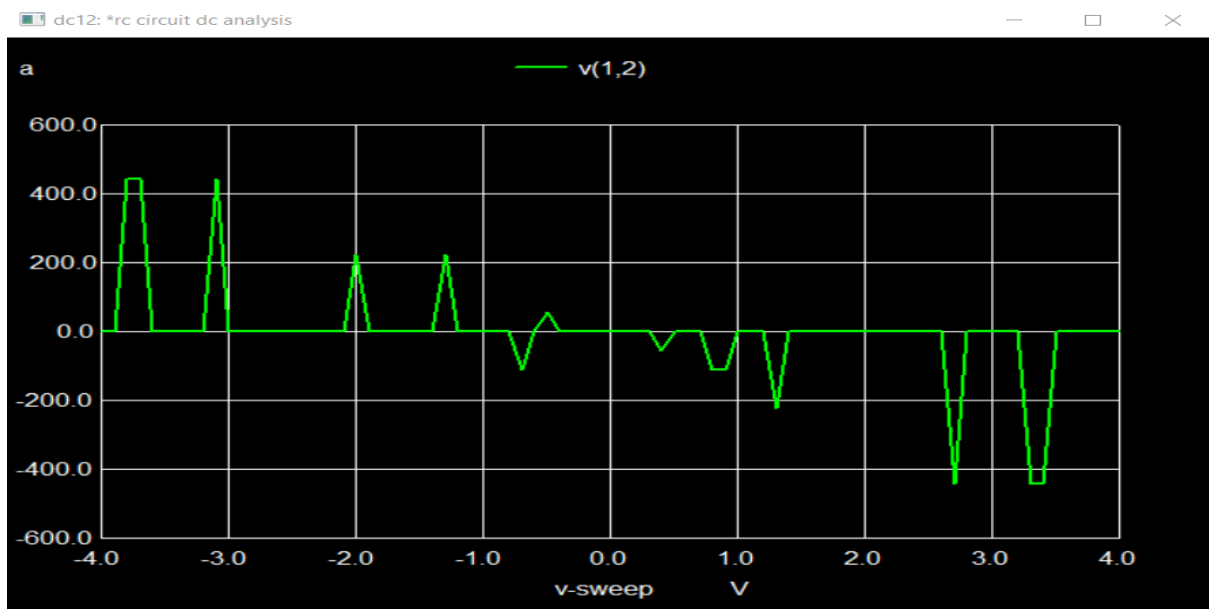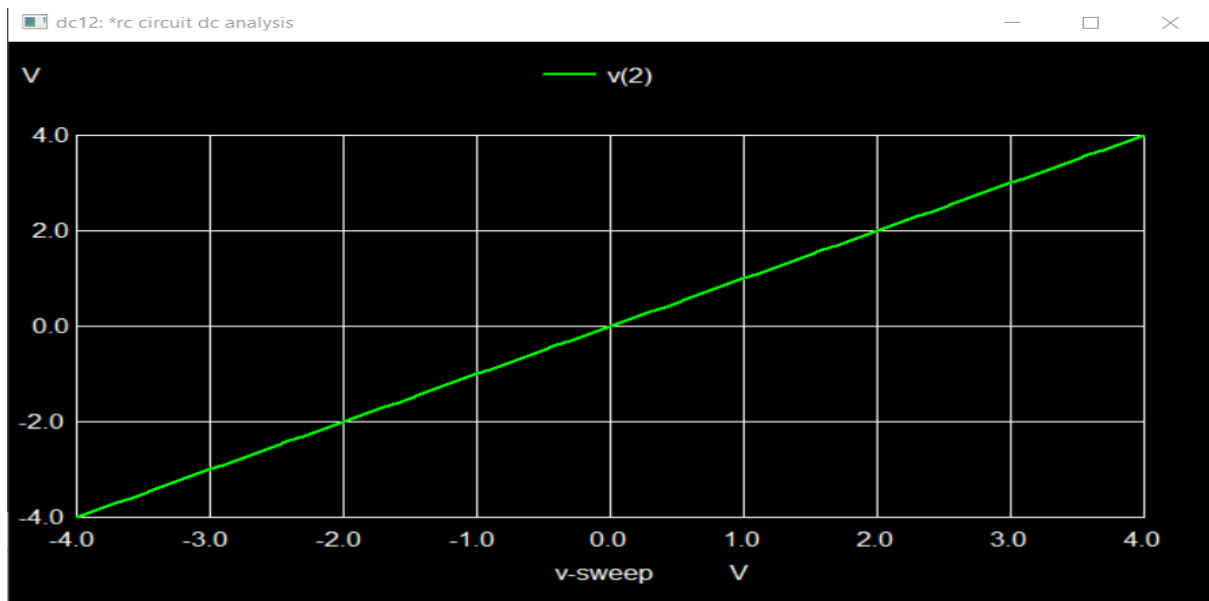

## CONCLUSION –

In the above DC analysis of RC circuit, the output for V2 across the capacitor is observed which shows a linear response and output across resistance is plotted and a very less current is flowing through the circuit .

## Question – RC circuit AC analysis

### Code –

\*Simple RC circuit AC Analysis

```
R 1 2 10Meg
```

```
C 2 0 10pf
```

```
Vin 1 0 ac 1
```

```
.ac dec 10 0.1 10Meg
```

```
.control
```

```
run
```

```
plot vdb(2)
```


```
plot vp(2)
```

```
meas ac f_3db When vdb(2)=-3 cross=last
```

```
.endc
```

```
.end
```


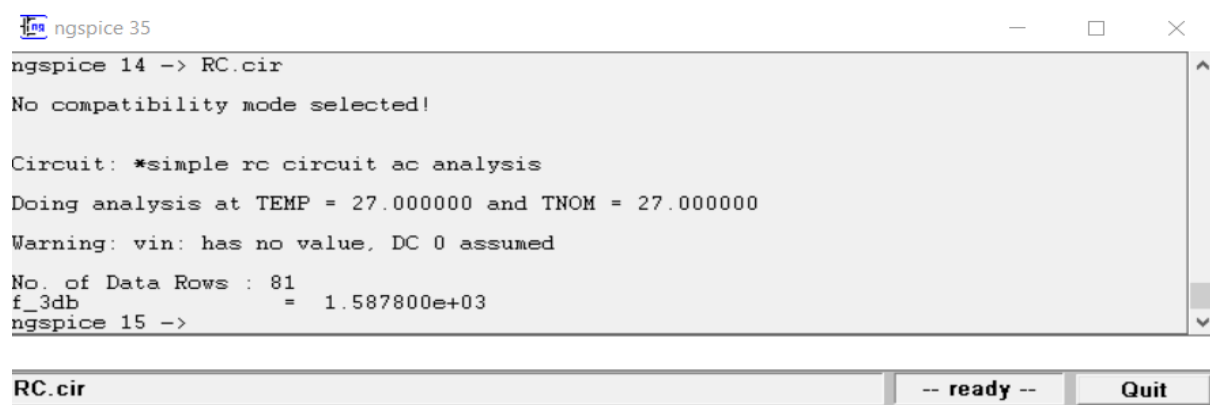
**Output – 3 dB frequency = 1.587800e+03 Hz**



```
ngspice 35
ngspice 14 -> RC.cir
No compatibility mode selected!

Circuit: *simple rc circuit ac analysis
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: vin: has no value, DC 0 assumed
No. of Data Rows : 81
f_3db              = 1.587800e+03
ngspice 15 ->
```

RC.cir -- ready -- Quit

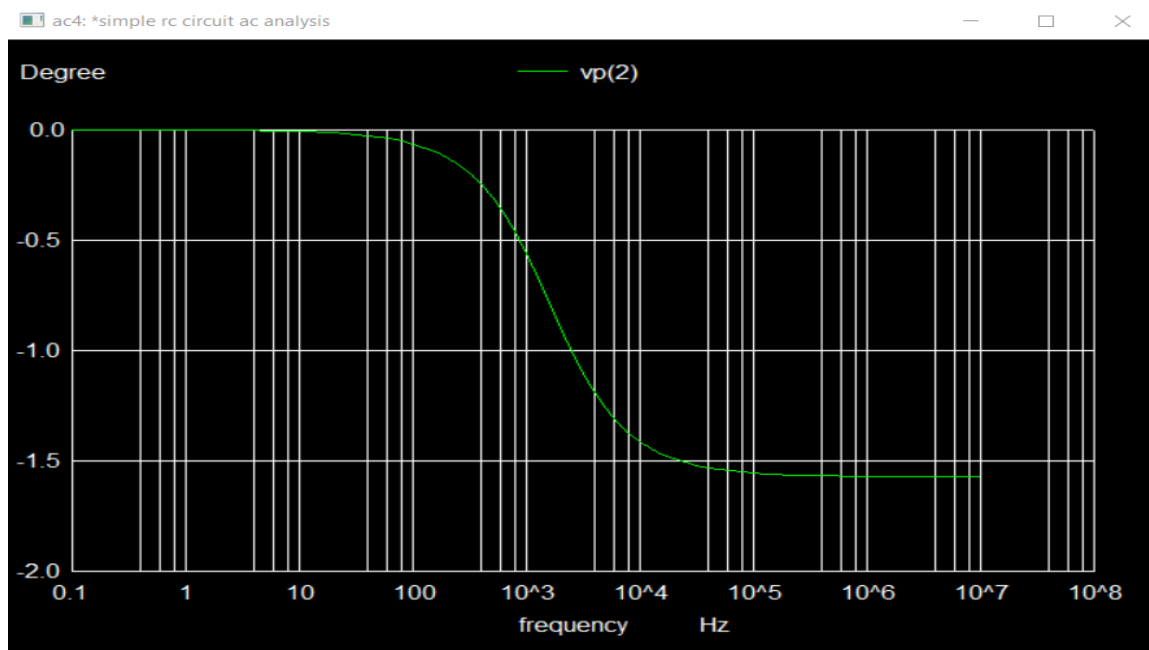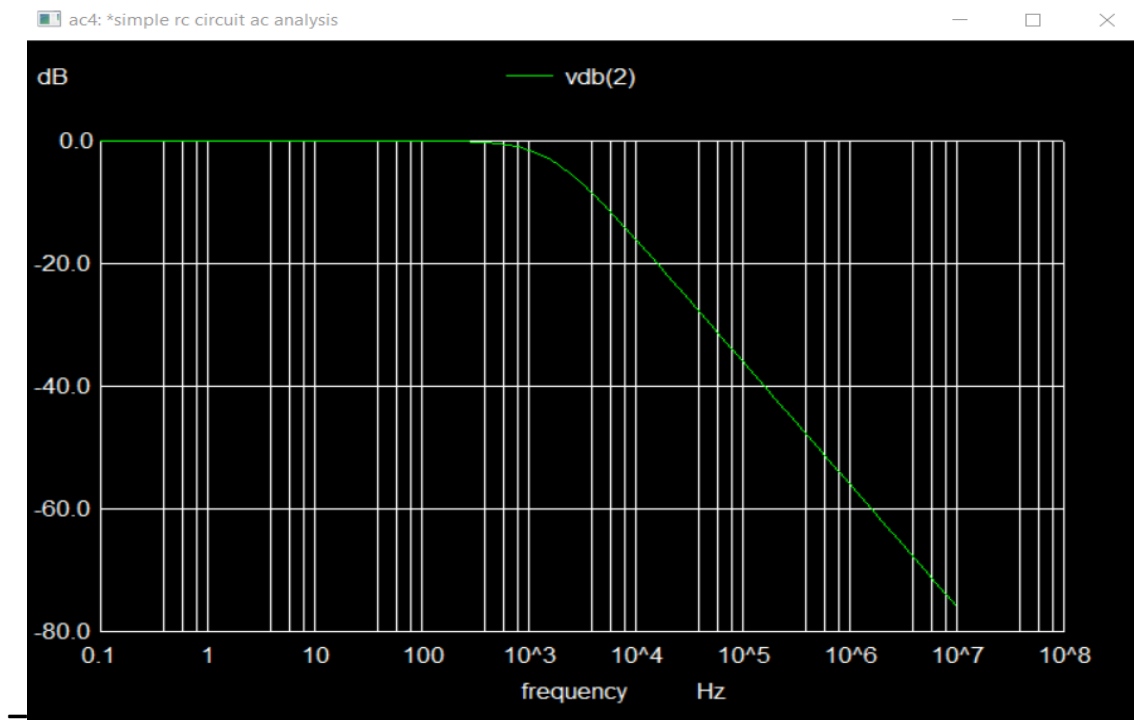


## Conclusion –

From the above AC analysis of RC circuit, I observed the frequency response across the capacitor as magnitude plot and phase plot in which I found the cut-off frequency as 1587.8 Hz

## Question – RC circuit Transient Analysis

### Circuit –

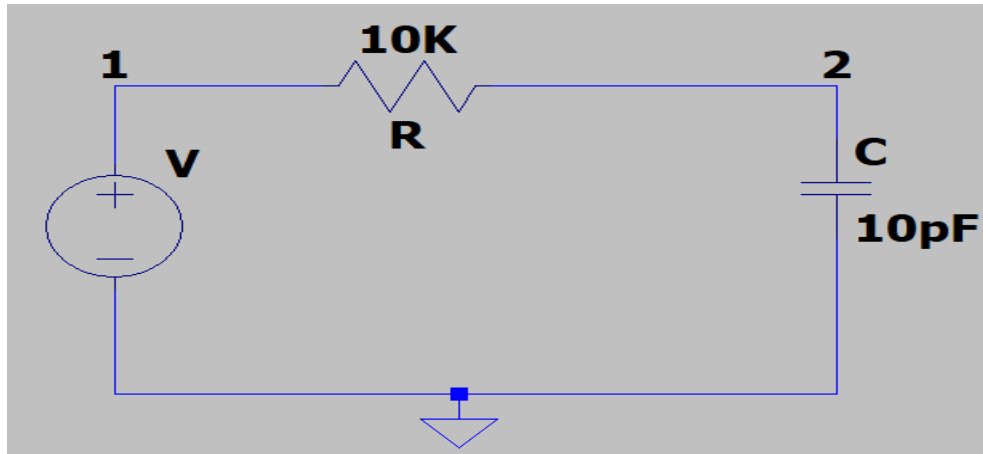




### Code –


```
R 1 2 10k
C 2 gnd 10p
V 1 gnd dc 0 pulse(0 1 1u 1p 1p 2u 1)
.tran 2ns 5us
.control
run
plot v(1)
plot v(2)
plot v(1,2)
plot i(v)
meas tran Rise_time trig v(2) val=0.1 rise=1 targ v(2) val=0.9 rise=1
print Rise_time
meas tran Fall_time trig v(2) val=0.9 fall=1 targ v(2) val=0.9 fall=1
print Fall_time
.endc
.end
```
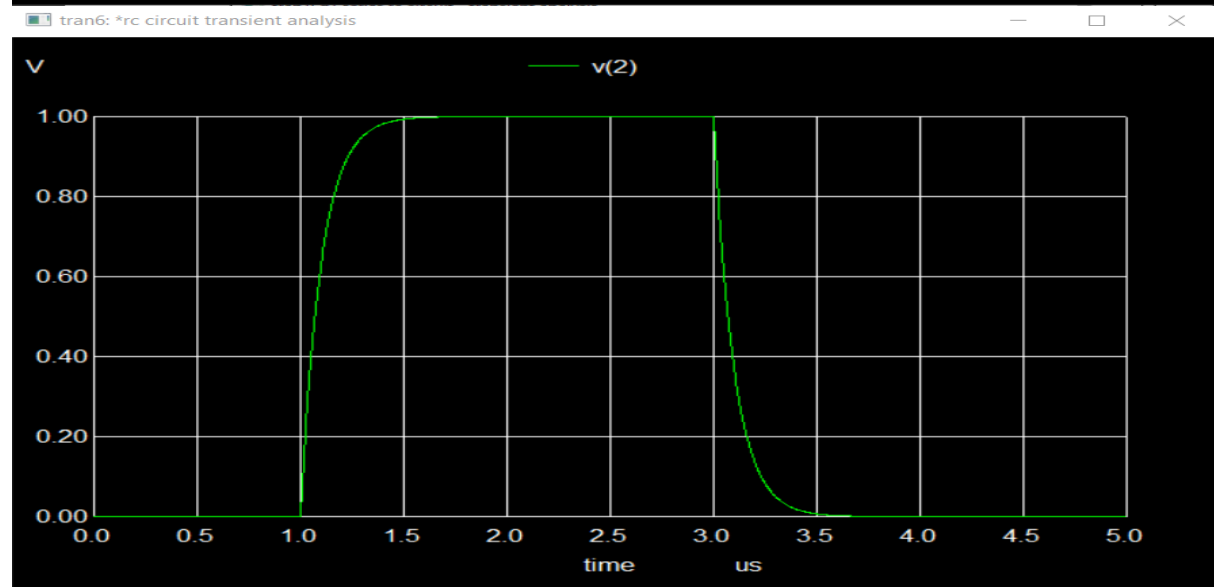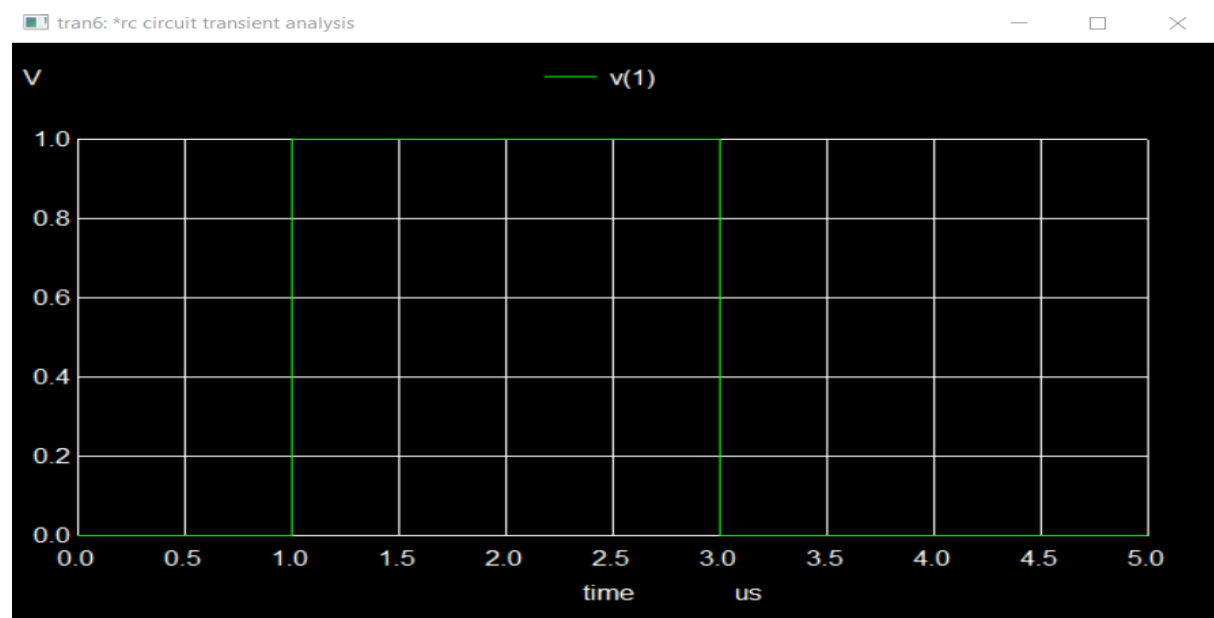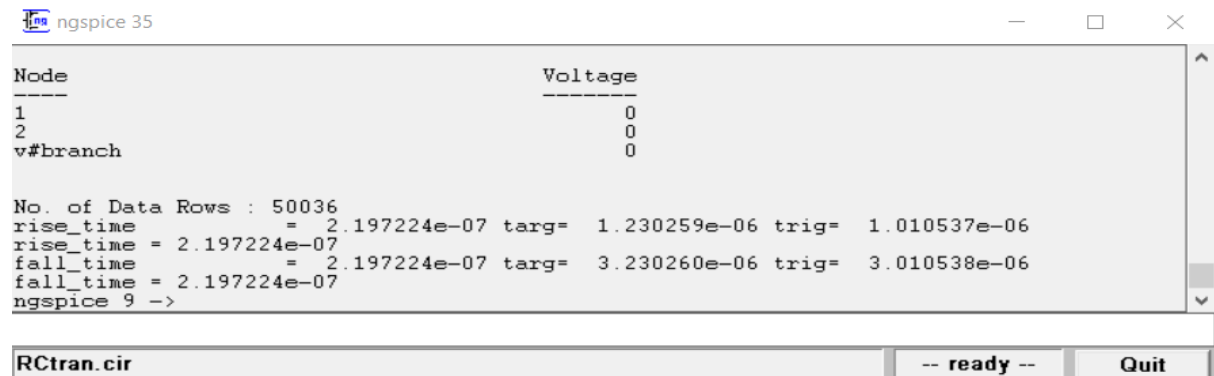
## Output –

Rise time =  $2.197224 \times 10^{-7}$  s

Fall time =  $2.197224 \times 10^{-7}$  s



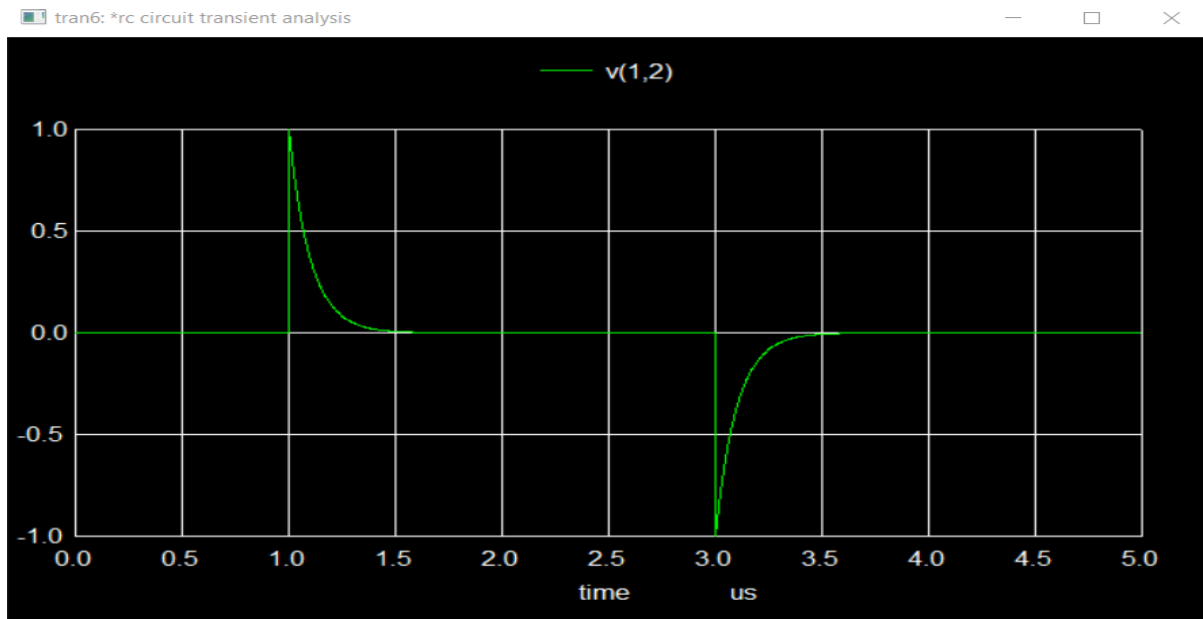


**Conclusion** – From the above AC transient analysis,

- I plotted the transient response across the capacitor and found the value of **rise time & fall time** about **0.22uSec** .
- In ac analysis of RC circuit, magnitude response and phase response across the capacitor is plotted in which the cut-off frequency(3 dB) measured as 1587.8Hz .

**Q (2). For simple RLC series circuit**

**Question** – DC analysis of RLC series circuit

**Circuit** –

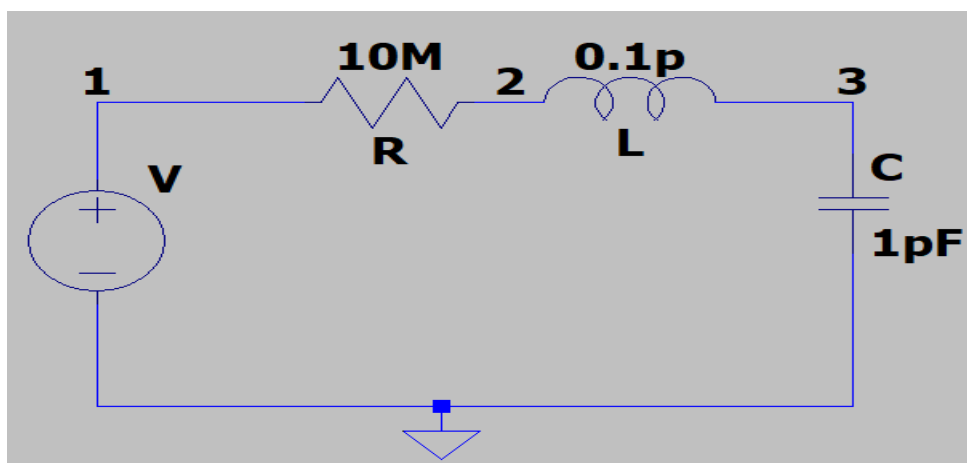



### Code –

\*Simple RLC circuit DC Analysis

```
R 1 2 10Meg
```

```
L 2 3 0.1p
```

```
C 3 0 1p
```

```
Vin 1 0 dc 0
```

```
.dc vin -5 5 0.1
```

```
.control
```

```
run
```

```
plot v(3)
```


```
plot v(1,2)
```



```
plot i(vin)
```

```
.endc
```

```
.end
```

### Output –

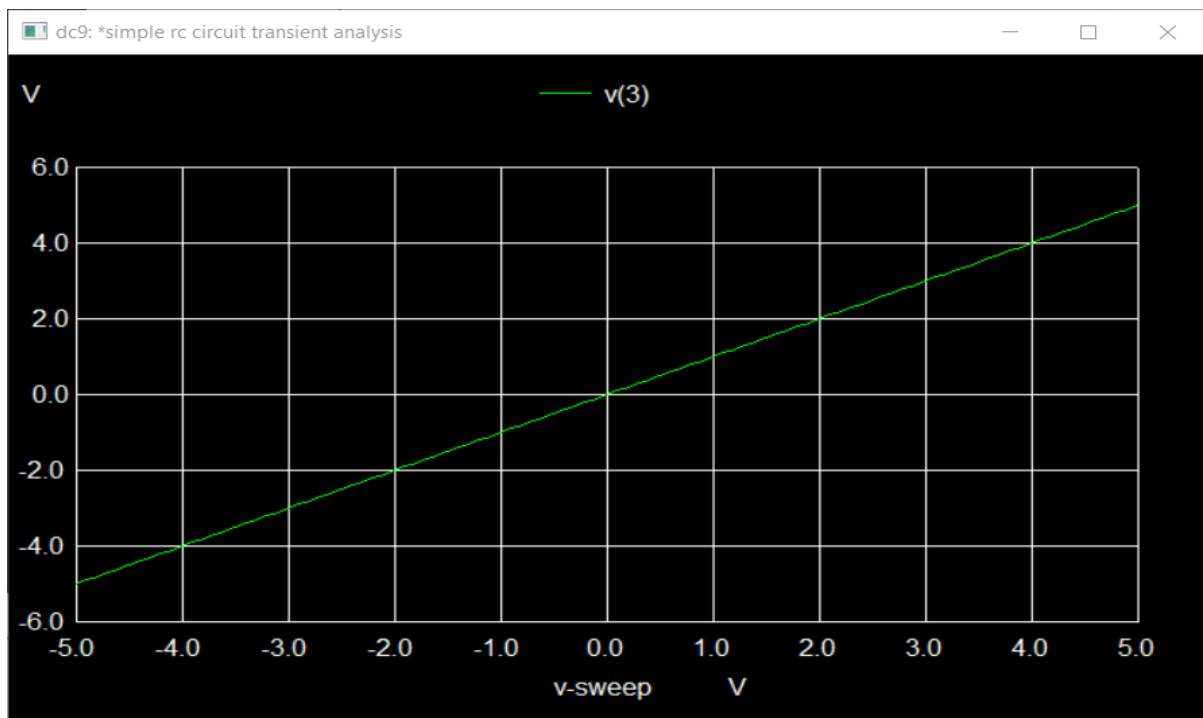

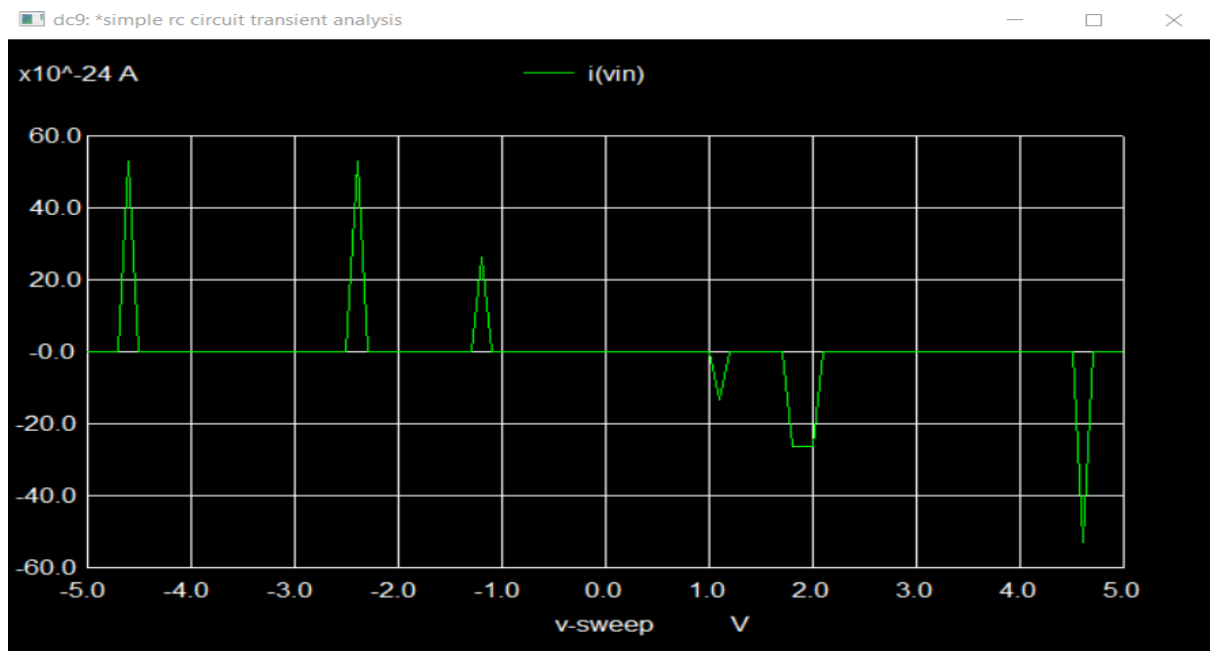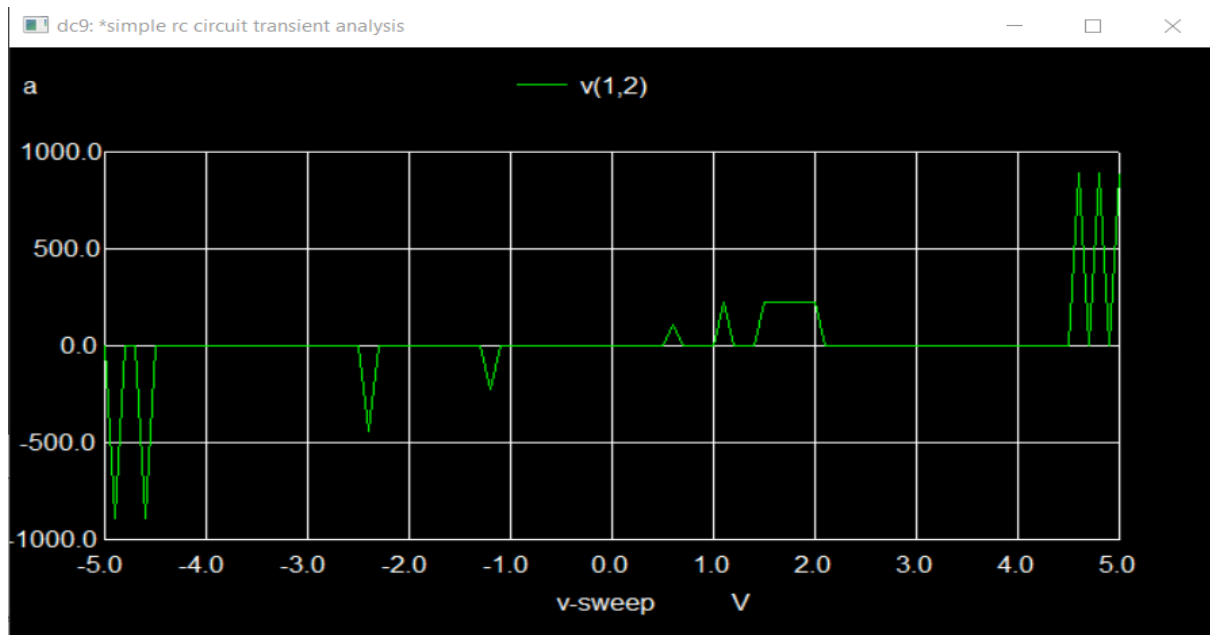

**Question – AC analysis of RLC series circuit**

**Code –**

\*Simple RLC circuit AC Analysis

R 1 2 10Meg

L 2 3 0.1p

C 3 0 1p

Vin 1 0 ac 1

.ac dec 1k 100 10Meg

.control

run

plot vdb(3) xlog

plot (57.26\*vp(3)) xlog

meas ac Cutoff\_Freq when vdb(3)=-3 cross=last

.endc


.end


**Output** – The cut-off frequency(3dB) =  $1.587775 \times 10^4$  Hz

```
ngspice 35
ngspice 1 -> RLCAC.cir
No compatibility mode selected!

Circuit: *simple rlc circuit ac analysis
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: vin: has no value, DC 0 assumed
No. of Data Rows : 5001
cutoff_freq      = 1.587775e+04
ngspice 2 ->
```

RLCAC.cir -- ready -- Quit

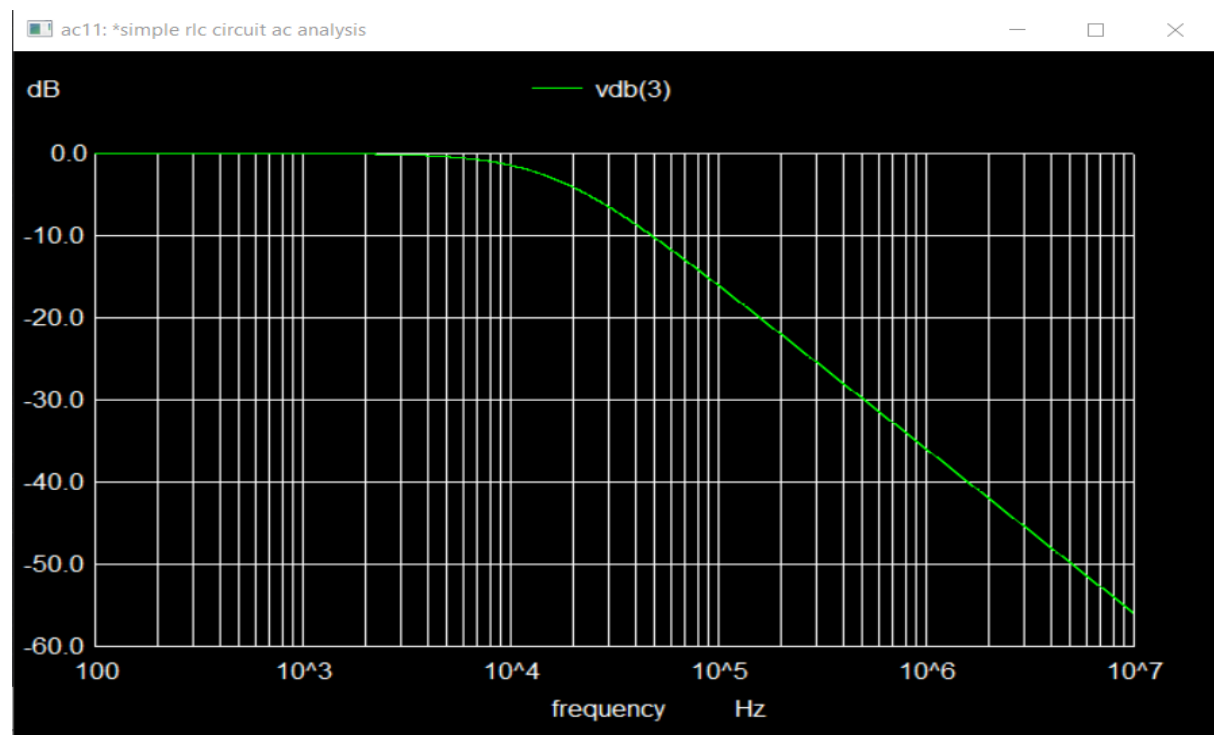

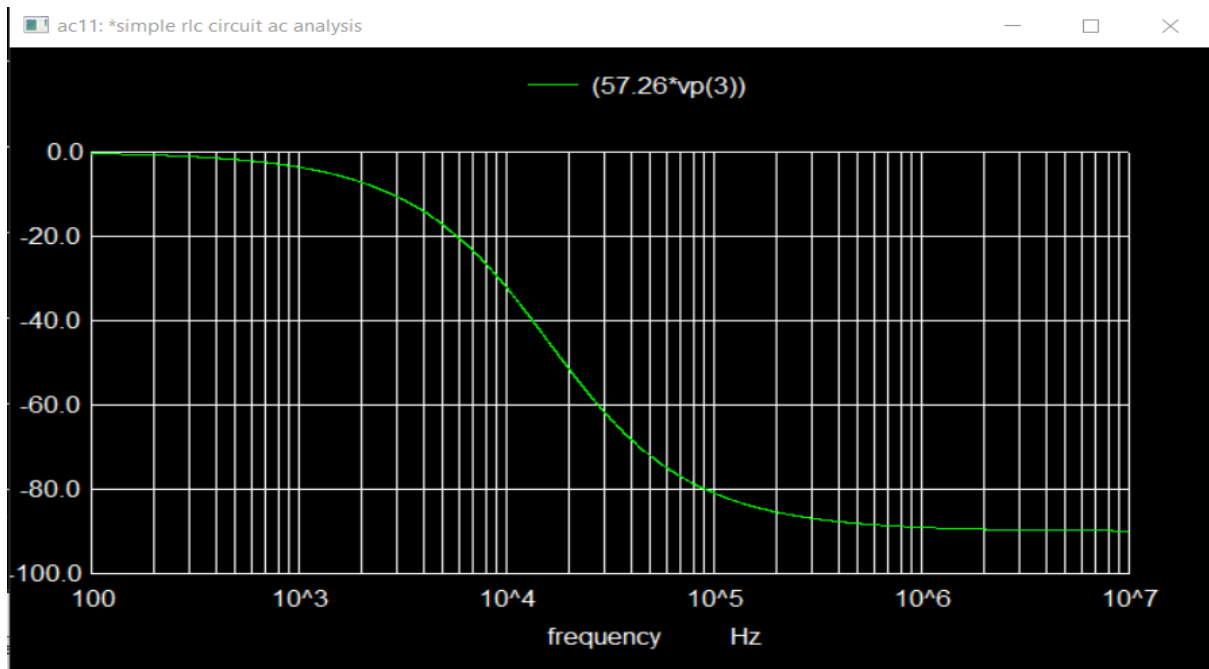

**Question** – Transient analysis of RLC series circuit

**Code** –

\*Simple RLC circuit Transient Analysis

R 1 2 10Meg

L 2 3 0.1p

C 3 0 1p

Vin 1 0 dc 0 pulse(0 1 10u 1p 1p 50u 1)

.tran 10n 100u

.control

run

plot v(1) v(3)

plot v(1,2)

plot i(vin)

meas tran Rise\_time trig v(3) val=0.1 rise=1 targ v(3) val=0.9 rise=1

print Rise\_time

meas tran Fall\_time trig v(3) val=0.9 fall=1 targ v(3) val=0.1 fall=1

```
print Fall_time
```

```
.endc
```


```
.end
```



**Output** – Rise time =  $2.197224 \times 10^{-5}$  s and Fall time =  $2.197224 \times 10^{-5}$  s

```
ngspice 35
-----
1          0
2          0
3          0
l#branch   0
vin#branch 0

No. of Data Rows : 10028
rise_time  = 2.197224e-05 targ= 3.302585e-05 trig= 1.105361e-05
rise_time  = 2.197224e-05
fall_time   = 2.197224e-05 targ= 8.295370e-05 trig= 6.098146e-05
fall_time   = 2.197224e-05
ngspice 18 ->

RLCtrans.cir  -- ready --  Quit
```

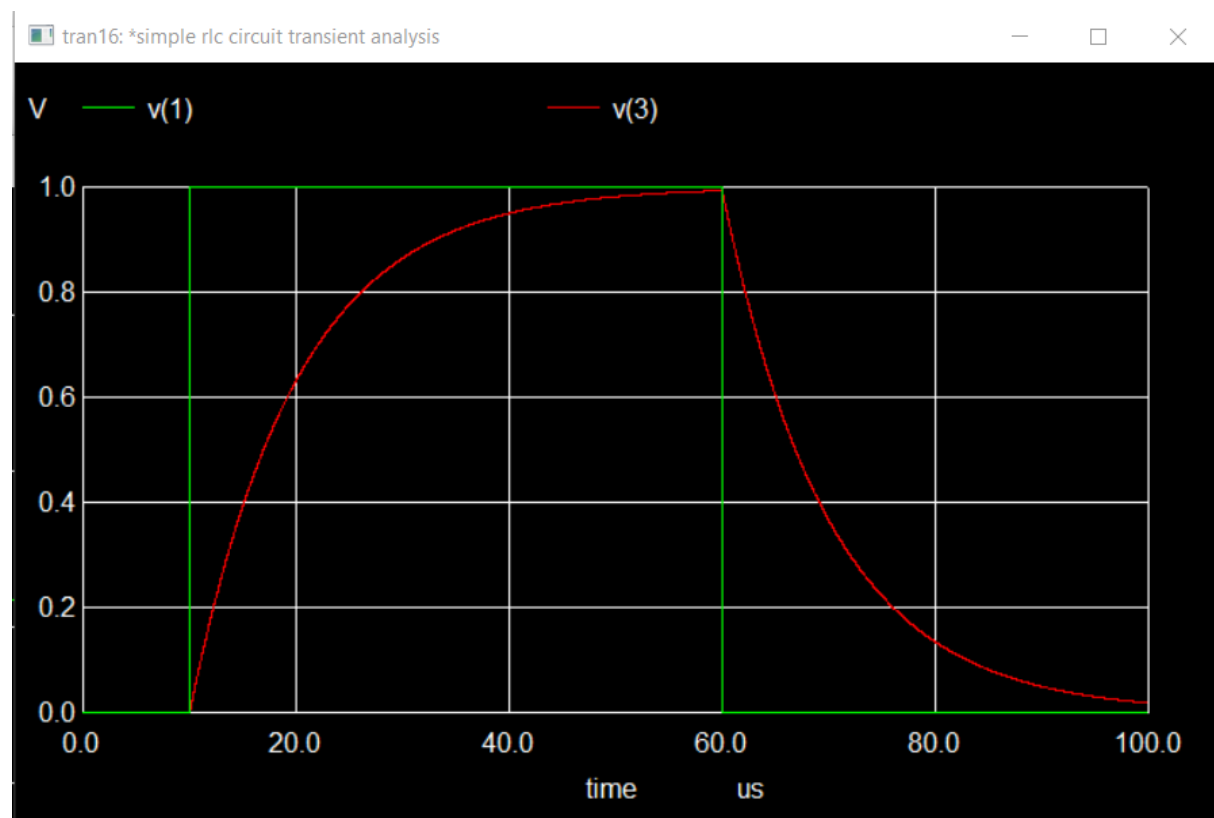

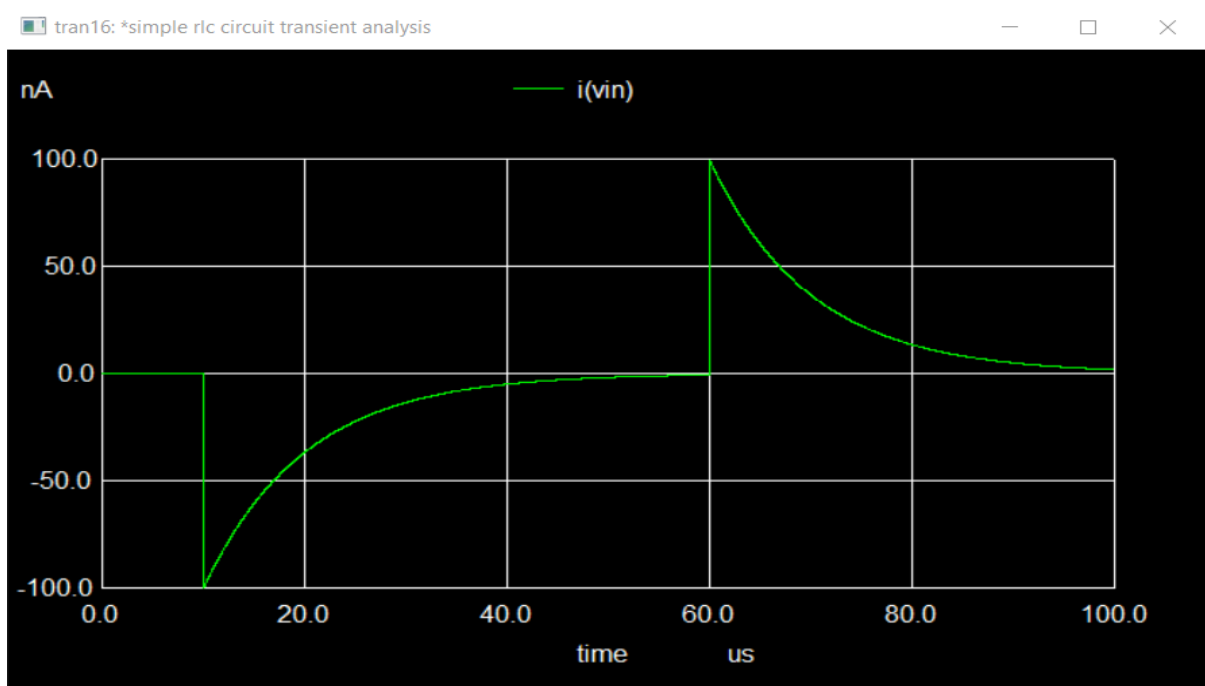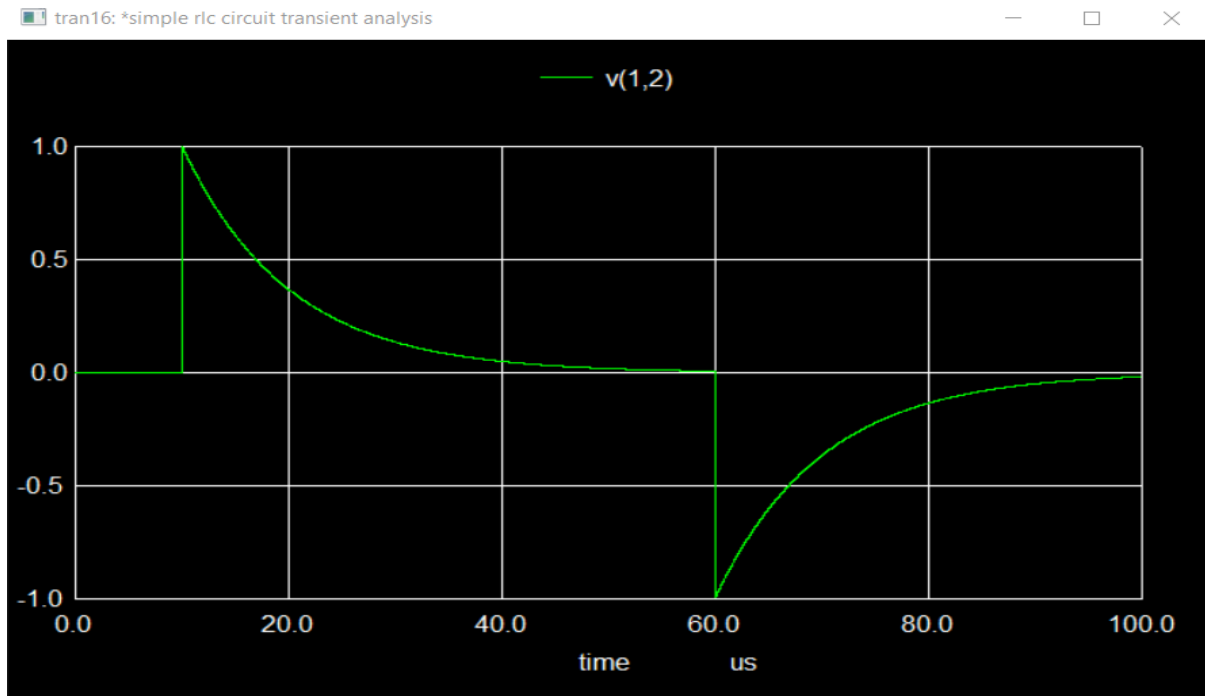

### Conclusion –

- In series RLC circuit DC analysis, the response across the output(capacitor) can be observed as linear response and a very less current is flowing through the circuit.
- In series RLC circuit AC analysis, the output is observed as magnitude and phase response in which the cut-off frequency found as 15877.75 Hz and a rise and fall time can be observed in transient analysis.